

# Physics 2102

## Lecture 8

### Capacitors II





# Capacitors in parallel and in series

- In parallel :

- $C_{eq} = C_1 + C_2$

- $V_{eq} = V_1 = V_2$

- $Q_{eq} = Q_1 + Q_2$

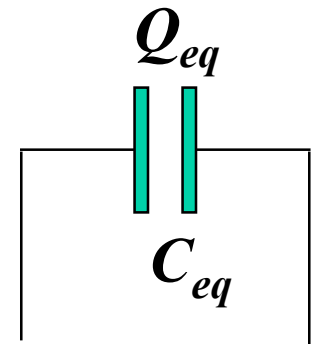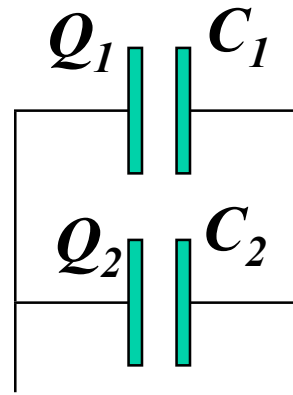


- In series :

- $1/C_{eq} = 1/C_1 + 1/C_2$

- $V_{eq} = V_1 + V_2$

- $Q_{eq} = Q_1 = Q_2$

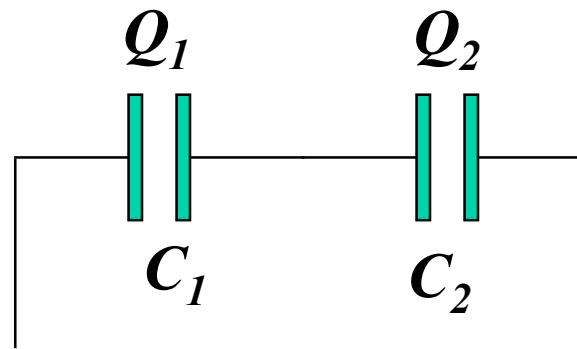


# Example 1

**What is the charge on each capacitor?**

- $Q = CV; V = 120 \text{ V}$
- $Q_1 = (10 \mu\text{F})(120\text{V}) = 1200 \mu\text{C}$
- $Q_2 = (20 \mu\text{F})(120\text{V}) = 2400 \mu\text{C}$
- $Q_3 = (30 \mu\text{F})(120\text{V}) = 3600 \mu\text{C}$

Note that:

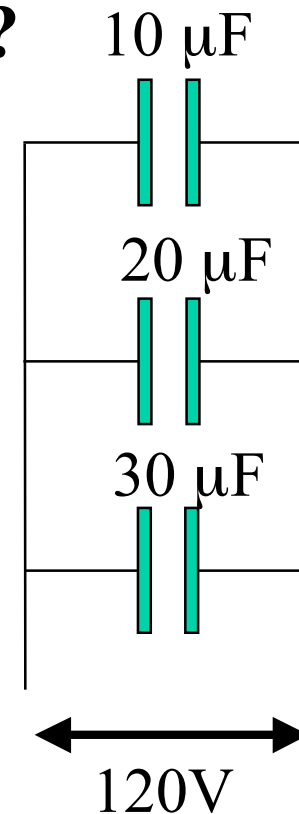- Total charge (7200  $\mu\text{C}$ ) is shared between the 3 capacitors in the ratio  $C_1:C_2:C_3$  — i.e. 1:2:3




## Example 2

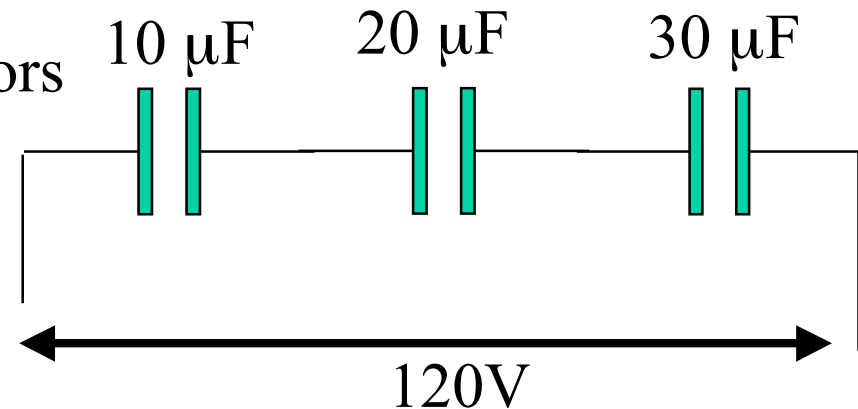**What is the potential difference across each capacitor?**

- $Q = CV$ ;  $Q$  is same for all capacitors
- Combined  $C$  is given by:

$$\frac{1}{C_{eq}} = \frac{1}{(10\mu F)} + \frac{1}{(20\mu F)} + \frac{1}{(30\mu F)}$$




- $C_{eq} = 5.46 \mu F$
- $Q = CV = (5.46 \mu F)(120V) = 655 \mu C$
- $V_1 = Q/C_1 = (655 \mu C)/(10 \mu F) = 65.5 V$
- $V_2 = Q/C_2 = (655 \mu C)/(20 \mu F) = 32.75 V$
- $V_3 = Q/C_3 = (655 \mu C)/(30 \mu F) = 21.8 V$

Note: 120V is shared in the ratio of INVERSE capacitances  
i.e.  $1:(1/2):(1/3)$   
(largest  $C$  gets smallest  $V$ )
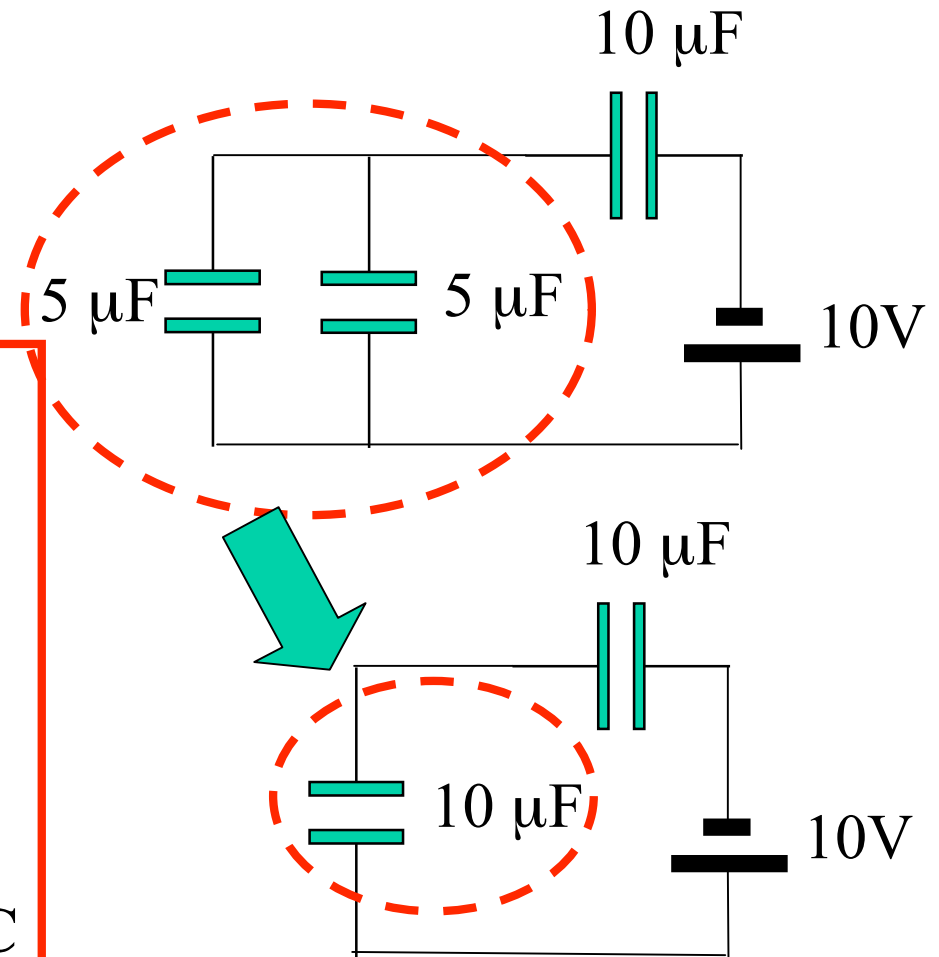
## Example 3


In the circuit shown, what is the charge on the  $10\mu\text{F}$  capacitor?

- The two  $5\mu\text{F}$  capacitors are in parallel
- Replace by  $10\mu\text{F}$
- Then, we have two  $10\mu\text{F}$  capacitors in series
- So, there is  $5\text{V}$  across the  $10\mu\text{F}$  capacitor of interest
- Hence,  $Q = (10\mu\text{F})(5\text{V}) = 50\mu\text{C}$


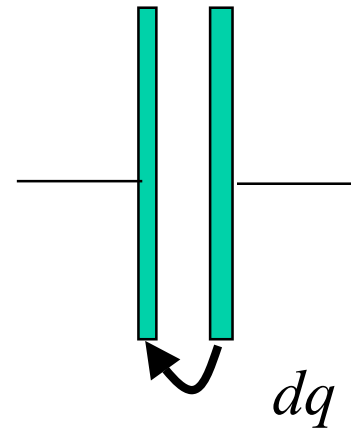
# Energy Stored in a Capacitor

- Start out with uncharged capacitor
- Transfer small amount of charge  $dq$  from one plate to the other until charge on each plate has magnitude  $Q$
- How much work was needed?



$$U = \int_0^Q V dq = \int_0^Q \frac{q}{C} dq = \frac{Q^2}{2C} = \frac{CV^2}{2}$$

# Energy Stored in Electric Field

- Energy stored in capacitor:  $U = Q^2/(2C) = CV^2/2$
- View the energy as stored in **ELECTRIC FIELD**
- For example, parallel plate capacitor:  
**Energy DENSITY** = energy/volume =  $u =$


$$U = \frac{Q^2}{2CAd} = \frac{Q^2}{2\left(\frac{\epsilon_0 A}{d}\right)Ad} = \frac{Q^2}{2\epsilon_0 A^2} = \frac{\epsilon_0}{2} \left(\frac{Q}{\epsilon_0 A}\right)^2 = \frac{\epsilon_0 E^2}{2}$$

volume =  $Ad$

General  
expression for  
any region with  
vacuum (or air)
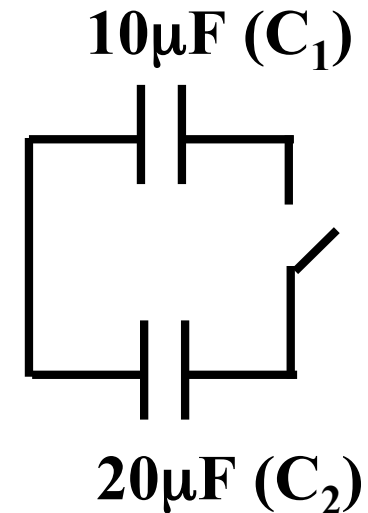
## Example

- $10\mu\text{F}$  capacitor is initially charged to  $120\text{V}$ .  $20\mu\text{F}$  capacitor is initially uncharged.
- Switch is closed, equilibrium is reached.
- How much energy is dissipated in the process?



Initial charge on  $10\mu\text{F} = (10\mu\text{F})(120\text{V}) = 1200\mu\text{C}$

After switch is closed, let charges =  $Q_1$  and  $Q_2$ .

Charge is conserved:  $Q_1 + Q_2 = 1200\mu\text{C}$

Also,  $V_{\text{final}}$  is same:  $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \Rightarrow Q_1 = \frac{Q_2}{2}$

- $Q_1 = 400\mu\text{C}$
- $Q_2 = 800\mu\text{C}$
- $V_{\text{final}} = Q_1/C_1 = 40\text{V}$


Initial energy stored =  $(1/2)C_1V_{\text{initial}}^2 = (0.5)(10\mu\text{F})(120)^2 = 72\text{mJ}$

Final energy stored =  $(1/2)(C_1 + C_2)V_{\text{final}}^2 = (0.5)(30\mu\text{F})(40)^2 = 24\text{mJ}$

Energy lost (dissipated) =  $48\text{mJ}$

# Dielectric Constant

*DIELECTRIC*

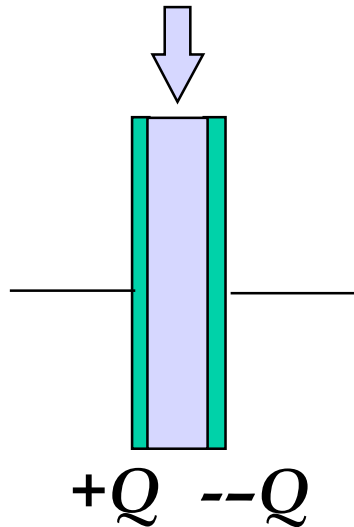


$$C = \kappa \epsilon_0 A/d$$

- If the space between capacitor plates is filled by a dielectric, the capacitance **INCREASES** by a factor  $\kappa$
- This is a useful, working definition for dielectric constant.
- Typical values of  $\kappa$  are 10–200

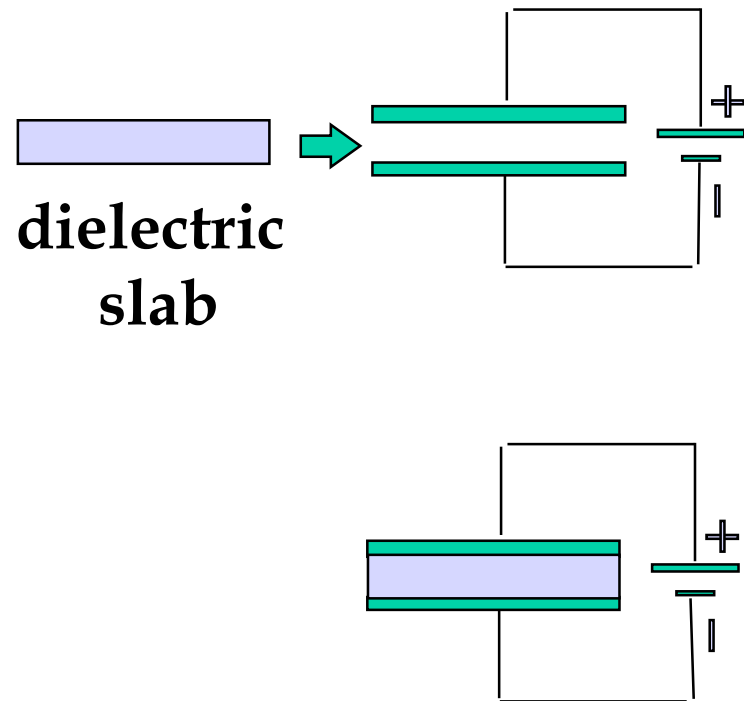
# Example

- Capacitor has charge  $Q$ , voltage  $V$
- Battery remains connected while dielectric slab is inserted.
- Do the following increase, decrease or stay the same:
  - Potential difference?
  - Capacitance?
  - Charge?
  - Electric field?


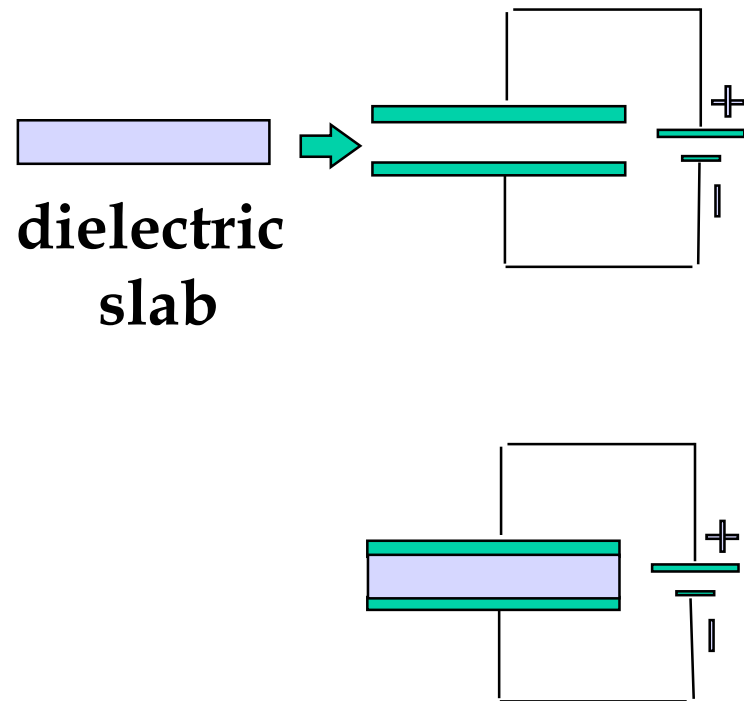
# Example

- Initial values:  
capacitance =  $C$ ; charge =  $Q$ ;  
potential difference =  $V$ ;  
electric field =  $E$ ;
- Battery remains connected
- $V$  is FIXED;  $V_{new} = V$  (**same**)
- $C_{new} = \kappa C$  (**increases**)
- $Q_{new} = (\kappa C)V = \kappa Q$  (**increases**).
- Since  $V_{new} = V$ ,  $E_{new} = E$  (**same**)



Energy stored?  $u = \epsilon_0 E^2 / 2 \Rightarrow u = \kappa \epsilon_0 E^2 / 2 = \epsilon E^2 / 2$

# Summary

- Any two charged conductors form a capacitor.
- Capacitance :  $C = Q/V$
- Simple Capacitors:
  - Parallel plates*:  $C = \epsilon_0 A/d$
  - Spherical* :  $C = 4\pi \epsilon_0 ab/(b-a)$
  - Cylindrical*:  $C = 2\pi \epsilon_0 L/\ln(b/a)$
- Capacitors in series: same charge, not necessarily equal potential; equivalent capacitance  $1/C_{eq} = 1/C_1 + 1/C_2 + \dots$
- Capacitors in parallel: same potential; not necessarily same charge; equivalent capacitance  $C_{eq} = C_1 + C_2 + \dots$
- Energy in a capacitor:  $U = Q^2/2C = CV^2/2$ ; energy density  $u = \epsilon_0 E^2/2$
- Capacitor with a dielectric: capacitance increases  $C' = \kappa C$